 


PROIECT

CIRCUITE INTEGRALE DIGITALE

Automatul de tranzitie



Bistabil D


A.

r	clk	Action
1	x	Reset
0		$Q^+ = D$
otherwise		Wait

Rezolvarea proiectului pe hartie

Proiect Circuite integrate digitale





Automatul de tranziție

 

Bitabil D

n	clk	Action
1	X	Reset
0	5	$Q^+ = D$
otherwise		Wait

Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	1	1	1
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	0	1

  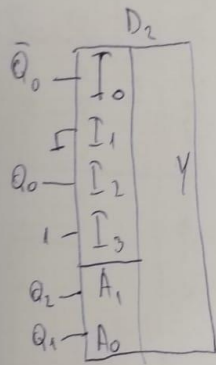 

Sursa de design pentru MUX4:1

```
35
36 entity mux4 is
37     Port ( i0 : in STD_LOGIC;
38           i1 : in STD_LOGIC;
39           i2 : in STD_LOGIC;
40           i3 : in STD_LOGIC;
41           a1 : in STD_LOGIC;
42           a0 : in STD_LOGIC;
43           y : out STD_LOGIC);
44 end mux4;
45
46 architecture Behavioral of mux4 is
47
48     signal a:std_logic_vector(1 downto 0);
49
50
51     begin
52         a <= a1 & a0;
53
54     process (i0, i1, i2, i3,  a)
55     begin
56         if a ="00" then
57             y<= i0;
58         elsif a= "01" then
59             y <=i1;
60         elsif a ="10" then
61             y<=i2;
62         elsif a="11" then
63             y<=i3;
64         end if;
65     end process;
```

Sursa de simulare MUX4:1


C:/Temp/project_1/project_1.srscs/sim_1/new/mux4_TB.vhd



```
37
38 architecture Behavioral of mux4_TB is
39 component mux4 is
40     Port ( i0 : in STD_LOGIC;
41           i1 : in STD_LOGIC;
42           i2 : in STD_LOGIC;
43           i3 : in STD_LOGIC;
44           a1 : in STD_LOGIC;
45           a0 : in STD_LOGIC;
46           y : out STD_LOGIC);
47 end component mux4;
48
49 signal i0, i1, i2, i3, a1, a0, y:std_logic;
50
51 begin
52
53     UUT: mux4 port map (i0 => i0, i1 => i1, i2 => i2, i3 => i3, a1 => a1, a0 => a0, y => y);
54
55 generate_i0:process
56 begin
57     i0 <= '0'; wait for 1 ns;
58     i0 <= '1'; wait for 1 ns;
59 end process;
60
61 generate_i1:process
62 begin
63     i1 <= '0'; wait for 2 ns;
64     i1 <= '1'; wait for 2 ns;
65 end process;
66
67 generate_i2:process
68 begin
```


Tel Console Messages Log Reports Design Run

C:/Temp/project_1/project_1.srscs/sim_1/new/mux4_TB.vhd



```
58 i0 <= '1'; wait for 1 ns;
59 end process;
60
61 generate_i1:process
62 begin
63 i1 <= '0'; wait for 2 ns;
64 i1 <= '1'; wait for 2 ns;
65 end process;
66
67 generate_i2:process
68 begin
69 i2 <= '0'; wait for 3 ns;
70 i2 <= '1'; wait for 3 ns;
71 end process;
72
73 generate_i3:process
74 begin
75 i3 <= '0'; wait for 1 ns;
76 i3 <= '1'; wait for 1 ns;
77 end process;
78
79 generate_a1:process
80 begin
81 a1 <= '0'; wait for 1 ns;
82 a1 <= '1'; wait for 1 ns;
83 end process;
84
85 generate_a0:process
86 begin
87 a0 <= '0'; wait for 2 ns;
88 a0 <= '1'; wait for 2 ns;
89 end process;
```

Simulare MUX4:1

 

Sursa de design bistabil




```
34  --use UNISIM.VComponents.all;
35
36  entity dff is
37      Port ( d : in STD_LOGIC;
38             clk : in STD_LOGIC;
39             r : in STD_LOGIC;
40             q : out STD_LOGIC;
41             qn : out STD_LOGIC);
42  end dff;
43
44  architecture Behavioral of dff is
45
46      signal qint:std_logic:='0';
47
48      begin
49
50      flipflop: process (r, clk)
51      begin
52          if r = '1' then
53              qint <= '0';
54          elsif rising_edge (clk) then
55              qint <= d;
56          else
57              qint <= qint;
58          end if;
59      end process;
60
61      q <= qint;
62      qn <= not qint;
63
64  end Behavioral;
65
```




Sursa de simulare Bistabil

C:/Temp/project_1/project_1.srscs/sim_1/new/dff_TB.vhd




```
33
34 entity dff_TB is
35   -- Port ( );
36 end dff_TB;
37
38 architecture Behavioral of dff_TB is
39   component dff is
40     Port ( d : in STD_LOGIC;
41           clk : in STD_LOGIC;
42           r : in STD_LOGIC;
43           q : out STD_LOGIC;
44           qn : out STD_LOGIC);
45   end component dff;
46
47   signal d, clk, r, q, qn:std_logic;
48
49   begin
50
51   uut: dff port map (d => d, clk => clk, r => r, q => q, qn => qn);
52
53   generate_d: process
54   begin
55     d <= '0'; wait for 2 ns;
56     d <= '1'; wait for 2 ns;
57   end process;
58
59   generate_clk: process
60   begin
61     clk <= '0'; wait for 1 ns;
62     clk <= '1'; wait for 1 ns;
63   end process;
64
```

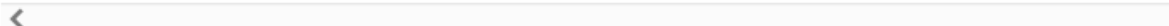

```
C:/Temp/project_1/project_1.srcs/sim_1/new/dff_TB.vhd

42         r : in STD_LOGIC;
43         q : out STD_LOGIC;
44         qn : out STD_LOGIC);
45     end component dff;
46
47     signal d, clk, r, q, qn:std_logic;
48
49     begin
50
51     uut: dff port map (d => d, clk => clk, r => r, q => q, qn => qn);
52
53     generate_d: process
54     begin
55         d <= '0'; wait for 2 ns;
56         d <= '1'; wait for 2 ns;
57     end process;
58
59     generate_clk: process
60     begin
61         clk <= '0'; wait for 1 ns;
62         clk <= '1'; wait for 1 ns;
63     end process;
64
65     generate_r: process
66     begin
67         r <= '0'; wait for 2 ns;
68         r <= '1'; wait for 2 ns;
69     end process;
70
71
72     end Behavioral;
73
```

Simulare Bistabil

 

Sursa de design automat


```
31  --library UNISIM;
32  --use UNISIM.VComponents.all;
33
34  entity automat is
35      Port ( r : in STD_LOGIC;
36            clk : in STD_LOGIC;
37            q : out STD_LOGIC_VECTOR (2 downto 0));
38  end automat;
39
40  architecture Behavioral of automat is
41      signal q2int, q1int, q0int, q0_neg, d2, d1, d0:std_logic;
42      signal qout:std_logic_vector(2 downto 0);
43
44      component dff is
45          Port ( d : in STD_LOGIC;
46                clk : in STD_LOGIC;
47                r : in STD_LOGIC;
48                q : out STD_LOGIC;
49                qn : out STD_LOGIC);
50  end component dff;
51
52      component mux4 is
53          Port ( i0 : in STD_LOGIC;
54                i1 : in STD_LOGIC;
55                i2 : in STD_LOGIC;
56                i3 : in STD_LOGIC;
57                a1 : in STD_LOGIC;
58                a0 : in STD_LOGIC;
59                y : out STD_LOGIC);
60  end component mux4;
61
62  begin
```

```

61
62 begin
63
64 U2: dff port map (d => d2,
65                   clk => clk,
66                   r => r,
67                   q => q2int);
68 U1: dff port map ( d => d1,
69                   clk => clk,
70                   r => r,
71                   q => q1int);
72 U0: dff port map ( d => d0,
73                   clk => clk,
74                   r => r,
75                   q => q0int);
76
77 M1: mux4 port map ( i0 => q0_neg, -- NOT q0int
78                   i1 => '0',
79                   i2 => q0int,
80                   i3 => '1',
81                   a1 => q2int,
82                   a0 => q1int,
83                   y => d2);
84 M2: mux4 port map ( i0 => q0_neg,
85                   i1 => '0',
86                   i2 => '1',
87                   i3 => '0',
88                   a1 => q2int,
89                   a0 => q1int,
90                   y => d1);
91 M3: mux4 port map ( i0 => q0_neg,
92                   i1 => '0',

```



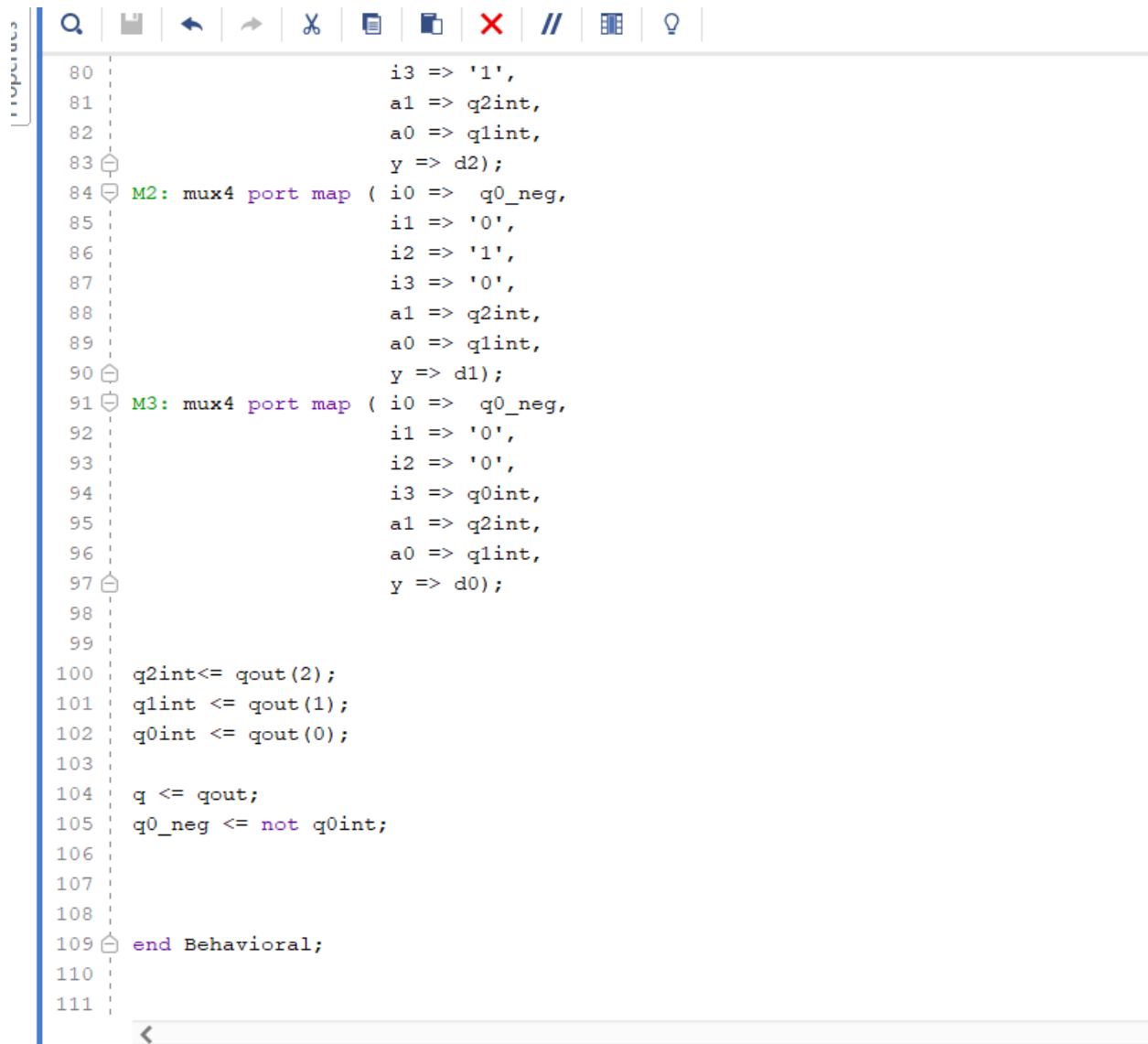

```
80         i3 => '1',
81         a1 => q2int,
82         a0 => qlint,
83         y => d2);
84 M2: mux4 port map ( i0 =>  q0_neg,
85                     i1 => '0',
86                     i2 => '1',
87                     i3 => '0',
88                     a1 => q2int,
89                     a0 => qlint,
90                     y => d1);
91 M3: mux4 port map ( i0 =>  q0_neg,
92                     i1 => '0',
93                     i2 => '0',
94                     i3 => q0int,
95                     a1 => q2int,
96                     a0 => qlint,
97                     y => d0);
98
99
100 q2int<= qout(2);
101 qlint <= qout(1);
102 q0int <= qout(0);
103
104 q <= qout;
105 q0_neg <= not q0int;
106
107
108
109 end Behavioral;
110
111
```

Sursa de simulare automat

Q

←

→

✂

✖

//

35

36

37

38

39

40

41

42

43

44

45

46

47

48

49

50

51

52

53

54

55

56

57

58

entity tb is

-- Port ();

end tb;

architecture Behavioral of tb is

component automat is

Port (r : in STD_LOGIC;

clk : in STD_LOGIC;

q : out STD_LOGIC_VECTOR (2 downto 0));

end component automat;

signal clk, r:std_logic;

signal q:std_logic_vector(2 downto 0);

begin

UUT: automat port map (clk => clk,

r => r,

q => q);

r <= '0' after 0 ns, '1' after 3 ns, '0' after 5 ns, '1' after 8 ns;

process

←

```
50
51 begin
52 UUT: automat port map ( clk => clk,
53                         r => r,
54                         q => q);
55
56
57     r <= '0' after 0 ns, '1' after 3 ns, '0' after 5 ns, '1' after 8 ns;
58 process
59 begin
60     clk <= '0';
61     wait for 1 ns;
62     clk <= '1';
63     wait for 1 ns;
64 end process;
65
66
67
68 end Behavioral;
69
70
71
72
73
```

Simulare finala

